

Mark schemes

1	(a) current that is always in the same direction	1
	(b) total resistance = 30 (Ω)	1
	$V = 0.4 \times 30$	1
	12 (V)	1
	<i>allow 12 (V) with no working shown for 3 marks an answer of 8 (V) or 4 (V) gains 2 marks only</i>	
	(c) $P = 0.4 \times 12 = 4.8$	1
	5 (W)	1
	<i>allow 5 (W) with no working shown for 2 marks allow 4.8 (W) with no working shown for 1 mark</i>	
		[6]
2	(a) battery, lamp and ammeter connected in series with variable resistor	1
	voltmeter in parallel with (filament) lamp	1
	(b) Level 2 (3–4 marks): A detailed and coherent description of a plan covering all the major steps is provided. The steps are set out in a logical manner that could be followed by another person to obtain valid results.	
	Level 1 (1–2 marks): Simple statements relating to relevant apparatus or steps are made but they may not be in a logical order. The plan would not allow another person to obtain valid results.	
	0 marks: No relevant content	
	Indicative content	
	<ul style="list-style-type: none"> • ammeter used to measure current • voltmeter used to measure potential difference • resistance of variable resistor altered to change current in circuit or change potential difference (across filament lamp) • resistance (of filament lamp) calculated or $R = V / I$ statement • resistance calculated for a large enough range of different currents that would allow a valid conclusion about the relationship to be made 	4
	(c) (as current increases) resistance increases (at an increasing rate)	1

(d) any value between 6.3 and 6.9 (Ω)

1

(e) **A:** Filament lamp

1

B: Resistor at constant temperature

1

C: Diode

1

[11]

3

(a) $V = 0.10 \times 45$

1

4.5 (V)

1

(b) $R = 12 / 0.10$

1

total resistance = 120 (Ω)

1

$R = 120 - 105 = 15$ (Ω)

1

(c) (total) resistance decreases

1


(so) current increases

1

[7]

4

(a)

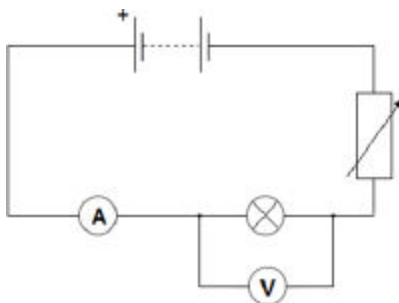

battery in series with bulb and ammeter

1

voltmeter in parallel with bulb

1

variable resistor

or

variable power pack

or

potentiometer

1

- (b) A is brighter because it has a higher current (than lamp B at any p.d.)

1

(therefore A has a) higher power output (than bulb B)

accept higher energy output per second

1

- (c) lower current (than lamp A) for the same potential difference

accept answer in terms of $R = V / I$

1

lower gradient (than lamp A)

1

- (d) 0 – 2 Volts

allow a range from 0 V up to any value between 1 and 2 V.

1

(for an ohmic conductor) current is directly proportional to potential difference

allow lines (of best fit) are straight and pass through the origin

1

(so) resistance is constant

1

[10]

5

- (a) (because the) potential of the live wire is 230 V

1

(and the) potential of the electrician is 0 V

1

(so there is a) large potential difference between live wire and electrician

1

charge / current passes through his body

allow voltage for potential difference

1

- (b) diameter between 3.50 and 3.55 (mm)

allow correct use of value of cross-sectional area of 9.5 to 9.9 (mm²) with no final answer given for 1 mark

2

- (c) $18000 = I \times 300$

1

$$I = 18000 / 300 = 60$$

1

$$13\,800 = (60^2) \times R$$

1

$$R = 13\,800 / 60^2$$

1

$$3.83 (\Omega)$$

1

allow 3.83(Ω) with no working shown for 5 marks

answer may also be correctly calculated using $P = IV$ and $V = IR$ if 230 V is used.

[11]

6

(a) (i) any **six** from:

- switch on
- read both ammeter and voltmeter
allow read the meters
- adjust variable resistor to change the current
- take further readings
- draw graph
- (of) V against I
allow take mean
- $R = V / I$
allow take the gradient of the graph

6

(ii) resistor would get hot if current left on

1

so its resistance would increase

1

(iii) 12 (V)

0.75 × 16 gains 1 mark

2

(iv) 15 (Ω)

1

16 is nearer to that value than any other

1

(b) if current is above 5 A / value of fuse

1

fuse melts

allow blows / breaks

*do **not** accept exploded*

1

breaks circuit

1
[15]

- 7** (a) attempt to draw four cells in series

1

correct circuit symbols

circuit symbol should show a long line and a short line, correctly joined together

example of correct circuit symbol:



1

- (b) (i) 6 (V)

allow **1** mark for correct substitution, ie

$$V = 3 \times 2 \text{ scores } \mathbf{1} \text{ mark}$$

provided no subsequent step

2

- (ii) 12 (V)

ecf from part (b)(i)

$$18 - 6$$

or

18 – their part (b)(i) scores **1** mark

2

- (iii) 9 (Ω)

ecf from part (b)(ii) correctly calculated

$$3 + \text{their part (b)(ii)} / 2$$

or

$$18 / 2 \text{ scores } \mathbf{1} \text{ mark}$$

provided no subsequent step

2

- (c) (i) need a.c.

1

battery is d.c.

1

- (ii) 3 (A)

allow **1** mark for correct substitution, ie

$$18 \times 2 = 12 \times I_s \text{ scores } \mathbf{1} \text{ mark}$$

2

[12]

- 8** (a) (i) live


1

- (ii) react faster 1
- (iii) live and neutral 1
- (b) (i) ammeter 1
- to measure current
accept to measure amps 1
- plus any **one** from:
- variable resistor (1)
to vary current (1)
accept variable power supply
accept change or control
 - *switch* (1)
to stop apparatus getting hot / protect battery
or
to reset equipment (1)
 - fuse (1)
to break circuit if current is too big (1)
- 2
- (ii) any **two** from:
- use smaller mass(es)
 - move mass closer to pivot
 - reduce gap between coil and rocker
 - more turns (on coil) *coil / loop*
 - iron core in coil
accept use smaller weight(s)
- 2

[9]

9

(a)

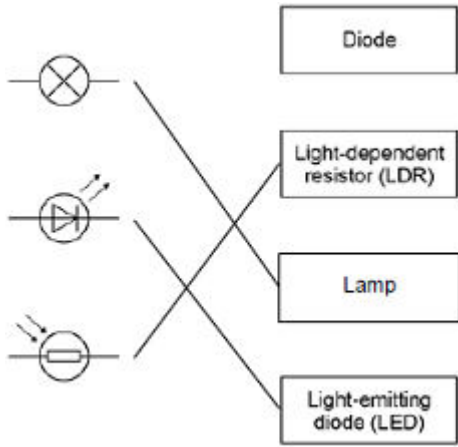

allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii) V_1

1

(c) (i) potential difference / voltage of the power supply

accept the power supply

accept the voltage / volts

accept number of cells / batteries

accept (same) cells / batteries

do not accept same ammeter / switch / wires

1

(ii) bar drawn – height 1.(00)A

ignore width of bar

allow 1 mark for bar shorter than 3rd bar

2


(iii) as the number of resistors increases the current decreases

1

[10]

10

(a) (i)

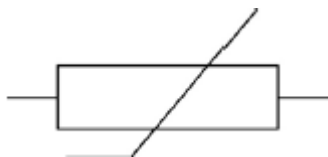


1

(ii) 360

allow 1 mark for correct substitution, ie $9 = 0.025 \times R$

2

(iii) sketch graph of correct shape, ie

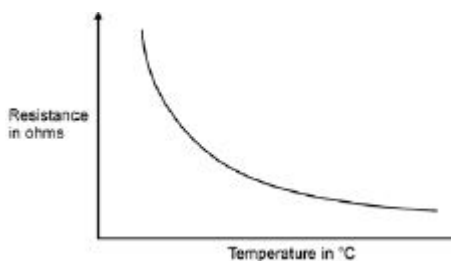

1

(iv) An automatic circuit to switch a heating system on and off.

1

(b) so ammeter reduces / affects current as little as possible

*accept so does not reduce / change the current (it is measuring)**accurate reading is insufficient**not change the resistance is insufficient*

1

(c) gives a common understanding

*accept is easier to share results**accept can compare results**do not need to be converted is insufficient**prevent errors is insufficient*

1

(d) replace Bunsen (and water) with a lamp

accept any way of changing light level

1

replace thermometer with light sensor

*accept any way of measuring a change in light level**datalogger alone is insufficient*

1

[9]

11

(a) decreases

1

(b) a filament bulb

allow bulb

1

an LED

1

- (c) Marks awarded for this answer will be determined by the Quality of Communication (QoC) as well as the standard of the scientific response.

0 marks

No relevant content.

Level 1 (1–2 marks)

There is a basic description of the method. This is incomplete and would not lead to any useful results.

Level 2 (3–4 marks)

There is a description of the method which is almost complete with a few minor omissions and would lead to some results.

Level 3 (5–6 marks)

There is a detailed description of the method which would lead to valid results. To gain full marks an answer including graph, or another appropriate representation of results, must be given.

examples of the physics points made in the response:

- read V and I
- read temperature
- apply heat
 - allow hot water to cool*
- read V and I at least one other temperature
- determine R from V / I
- range of temperatures above 50 °C

extra detail:

- use thermometer to read temperature at regular intervals of temperature
- remove source of heat and stir before taking readings
- details of attaining 0 °C or 100 °C
- last reading taken while boiling
- graph of R against T
- at least 3 different temperatures

6

- (d) (i) Q

1

- (ii) (80, 3.18)

1

- (iii) any **one** from:

- measurement of V too small
- measurement of I too big
- incorrect calculation of R
- thermometer misread

allow misread meter

ignore any references to an error that is systematic

1

(iv) any **two** from:

- not portable
allow requires a lot of equipment allow takes time to set up
- needs an electrical supply
- cannot be read directly
accept it is more difficult to read compared to liquid-in-glass

2

[14]

12

(a) (i) to obtain a range of p.d. values

- accept increase / decrease current / p.d. / voltage / resistance*
- accept to change / control the current / p.d. / voltage / resistance*
- to provide resistance is insufficient*
- a variable resistor is insufficient*
- do **not** accept electricity for current*

1

(ii) temperature of the bulb increases

- accept bulb gets hot(ter)*
- accept answers correctly*
- expressed in terms of collisions between (free) electrons and ions / atoms*
- bulb gets brighter is insufficient*

1

(iii) 36

- allow **1** mark for correct substitution, ie 12×3 provided no subsequent step shown*

2

watt(s) / W

- accept joules per second / J/s*
- do **not** accept w*

1

(b) Marks awarded for this answer will be determined by the Quality of Written Communication (QWC) as well as the standard of the scientific response. Examiners should also refer to the information in the [Marking guidance](#), and apply a 'best-fit' approach to the marking.

0 marks

No relevant content.

Level 1 (1-2 marks)

There is a basic comparison of either a cost aspect or an energy efficiency aspect.

Level 2 (3-4 marks)

There is a clear comparison of either the cost aspect or energy efficiency aspect

OR

a basic comparison of both cost and energy efficiency aspects.

Level 3 (5-6 marks)

There is a detailed comparison of both the cost aspect and the energy efficiency aspect.

For full marks the comparisons made should support a conclusion as to which type of bulb is preferable.

Examples of the points made in the response:**cost**

- halogen are cheaper to buy
simply giving cost figures is insufficient
- 6 halogen lamps cost the same as one LED
- LEDs last longer
- need to buy 18 / more halogen lamps to last the same time as one LED
- 18 halogens cost £35.10
- costs more to run a halogen than LED
- LED has lower maintenance cost (where many used, eg large departmental store lighting)

energy efficiency

- LED works using a smaller current
- LED wastes less energy
- LEDs are more efficient
- LED is 22% more energy efficient
- LED produces less heat
- LED requires smaller input (power) for same output (power)

6
[11]

13

(a) 35

*an answer with more than 2 sig figs that rounds to 35 gains 2 marks**allow 2 marks for correct method, ie $\frac{230}{6.5}$* *allow 1 mark for $I = 6.5$ (A) or $R = \frac{230}{26}$* *an answer 8.8 gains 2 marks**an answer with more than 2 sig figs that rounds to 8.8 gains 1 mark*

3

(b) (maximum) current exceeds maximum safe current for a 2.5 mm² wire*accept power exceeds maximum safe power for a 2.5 mm² wire***or**

(maximum) current exceeds 20 (A)

(maximum) current = 26 (A) is insufficient

1

a 2.5 mm² wire would overheat / melt*accept socket for wire**do **not** accept plug for wire*

1

(c) a.c. is constantly changing direction

*accept a.c. flows in two directions**accept a.c. changes direction**a.c. travels in different directions is insufficient*

1

d.c. flows in one direction only

1

[7]**14**

(a) 25(Ω)

1

(b) (i) 2(V)

allow 1 mark for showing a correct method, ie 6 / 3

2

(ii) equal to

1

[4]**15**

(a) (i) 50 (Hz)

1

(ii) 2760 (W)

1

(b) 12

allow 1 mark for correct substitution, ie 2400/200

or

allow 1 mark for 2760/230 provided no subsequent step shown

2

amps

1

(c) the charge is directly proportional to the time switched on for

accept for 1 mark the longer time (to boil), the greater amount of charge


or *positive correlation*

or *they are proportional*

2


[7]

16

(a) (i) symbol for a diode 

accept 

1

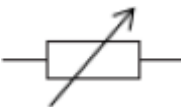symbol for a variable resistor 

1

(ii) voltmeter is in series **or** voltmeter is not in parallel

1

ammeter is in parallel **or** ammeter is not in series

*accept an answer in terms of how the circuit should be corrected
voltmeter and ammeter are wrong way around is insufficient*

1

(b) (i) 0.2 (V)

accept any value between 0.20 and 0.21 inclusive

1

(ii) 37.5

allow 1 mark for $I = 0.008$

or

allow 2 marks for correct substitution, ie $0.3 = 0.008 \times R$

or

*allow 1 mark for a correct substitution using $I = 0.8$ **or** $I = 0.08$*

or $I = 0.009$

or

*allow 2 marks for answers of 0.375 **or** 3.75 **or** 33(.3)*

3

- (c) (i) 25
allow 1 mark for obtaining period = 0.04(s) 2
- (ii) diode has large resistance in reverse / one direction 1
- so stops current flow in that / one direction
allow diodes only let current flow one way / direction
allow 1 mark for the diode has half-rectified the (a.c. power) supply 1
- [12]**
- 17** (a) (i) 50(Hz)
ignore any unit given 1
- (ii) any **two** from:
- (some) current flows to Earth
accept ground for Earth
 - current flows through copper braid
accept current flows through the earth wire
accept electricity for current in either the first or second marking point but not both
 - RCCB detects difference between current in live and neutral wire 2
- (iii) can be reset
accept does not need replacing
- or**
- faster acting
accept switches circuit off faster 1
- (b) (i) 79 200
allow 1 mark for correct substitution, ie $11 = \frac{Q}{2 \times 3600}$
an answer 22 gains 1 mark 2
- coulombs / C
*do **not** accept c* 1

- (ii) 18 216 000
accept for **2** marks 18 216 kJ **or** 18.216 MJ

or

- 230 × their (b)(i) correctly calculated
allow **1** mark for correct substitution, ie 230 × their (b)(i) **or**
allow **1** mark for power calculated as 2530(W)

2

- (c) increases temperature of thermistor

1

changes resistance (of thermistor)


do **not** accept increases resistance (of thermistor)
an answer decreases resistance (of thermistor) gains **2** marks

1

[11]

18


- (a) (i) ammeter symbol correct and drawn in series

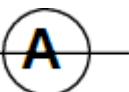accept 

do **not** accept lower case a

1

voltmeter symbol correct and drawn in parallel with the material

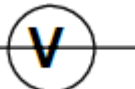do **not** accept 

1

- (ii) adjust / use the variable resistor
accept change the resistance

or

change the number of cells
accept battery for cell
accept change the pd / accept change the voltage
accept increase / decrease for change

1

- (b) (i) 37.5 (Ω)
accept answer between 36 and 39 inclusive

1

- (ii) 5.6(25) **or** their (b)(i) × 0.15
allow **1** mark for correct substitution ie 37.5 **or** their (b)(i) × 0.15
provided no subsequent step shown

2

- (c) (i) the thicker the putty the lower the resistance

*answer must be comparative
accept the converse*

1

- (ii) any **one** from:

- measuring length incorrectly
accept may be different length
- measuring current incorrectly
*do **not** accept different currents*
- measuring voltage incorrectly
*do **not** accept different voltage*
- ammeter / voltmeter incorrectly calibrated
- thickness of putty not uniform
*do **not** accept pieces of putty not the same unless qualified*
- meter has a zero error
*do **not** accept systematic / random error
accept any sensible source of error eg putty at different temperatures
do **not** accept human error without an explanation
do **not** accept amount of putty not same*

1

[8]

19

- (a) (i) 2

allow 1 mark for correct substitution i.e. 0.8×2.5 provided no further step shown

2

- (ii) straight line drawn from origin to 2, 0.8

or

their (a)(i), 0.8

1

curve from 2, 0.8 to 12,2

or

their (a)(i) 0.8 to 12,2

accept curve from 2, 0.9 to 12,2

or

their (a)(i) 0.9 to 12,2

'convex' curve required

accept a curve that flattens between 10 and 12V

1

- (iii) filament / lamp gets hot
accept temperature increases

1

- (b) 108

allow 1 mark for correct substitution i.e. 1.5×72 provided no further step shown

2

[7]

20

- (a) (i) 15

1

- (ii) 4.5 or their (a)(i) $\times 0.3$ correctly calculated

allow 1 mark for correct substitution, ie 0.3×15 /their (a)(i), provided no subsequent step

2

- (ii) decrease

1

- (b) **Y**

*accept any correct indication
reason only scores if **Y** is chosen
accept voltage for p.d.*

1

(only one that) shows a direct current / p.d.

or

a battery / cell gives a direct current

*accept both **X** and **Z** are a.c.*

or

a battery/cell gives a constant current/p.d.


*accept it's a constant current/p.d.
it is not changing is insufficient*

1

[6]

21

- (a) (i) correct symbol ringed

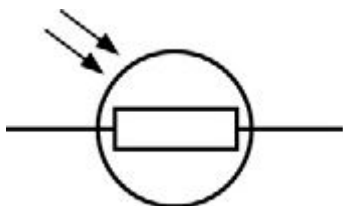

1

(ii) accept any suggestion that would change light intensity, eg:

- torch on or off
accept power of torch
*do **not** accept watts / wattage of torch*
- distance between torch and LDR
- lights in room on or off
- shadow over the LDR

1

(b) resistance decreases

1

from 600 k Ω to 200 k Ω

accept by 400 k Ω

1

(c) (i) no numbers for light intensity

or

light intensity is categoric / a description / not continuous

not enough results is insufficient

1

(ii) YES

mark is for the reason

both show that resistance increases with decreasing (light) intensity / brightness

accept they both get the same results / pattern

1

(d) A circuit that automatically switches outside lights on when it gets dark.

1

[7]

22

(a) electric current
(rate of) flow of (electric) charge / electrons

accept $I = \frac{Q}{t}$

with Q and t correctly named

1

potential difference

work done / energy transferred per coulomb of charge
(that passes between two points in a circuit)

$$\text{accept } V = \frac{W}{Q}$$

with W and Q correctly named

1

(b) metals contain free electrons (and ions)

accept mobile for free

1

as temperature of filament increases ions vibrate faster /
with a bigger amplitude

accept atoms for ions

accept ions/atoms gain energy

accept vibrate more for vibrate faster

do not accept start to vibrate

1

electrons collide more (frequently) with the ions

or

(drift) velocity of electrons decreases

do not accept start to collide

accept increasing the p.d. increases the temperature (1 mark)

and

(and) resistance increases with temperature (1 mark) if no other
marks scored

1

(c) 7.8

allow 1 mark for obtaining value 1.3 from graph

or allow 1 mark for a correct calculation using an incorrect current
in the range 1.2-1.6 inclusive

2

[7]

23

(a) (i) 50 000

allow 1 mark for correct substitution, ie

$$6 = 0.00012 \times R$$

$$\text{or } 6 = 0.12 \times R$$

or answers of 25 000 or 50 gain 1 mark

or allow 1 mark for an incorrect answer caused by one error only ie
using 3V or an incorrect conversion of current

2

ohm / Ω *an answer 50k Ω gains 3 marks*

1

(ii) (body) resistance changes

or

body fat/resistance affected by (many) factors

accept named factor, eg age, gender, height, fitness, bone structure, muscle, drinking water related to body fat / resistance

1

(iii) gives misleading / wrong/inaccurate value

do not credit if specifically linked to a change in mass / weight

1

(because) high water content changes body resistance

*accept a specific change to resistance**water changes body mass is insufficient*

1

(b) (i) RCCB – detects difference between current in live and neutral (wires)

accept RCCB can be reset

1

fuse – (overheats and) melts

accept blows for melts

1

(ii) switches the circuit / hedge trimmers off within 60 milliseconds

*allow for 1 mark the RCCB / it is (very) fast.**do not accept the bigger the current the faster the RCCB switches off*

2

[10]**24**

(a) (i) 6

1

(ii) variable resistor

1

(iii) voltmeter

1

(b) (i) point at 3 V ringed

1

(ii) The student misread the ammeter.

1

(iii) 1 (volt)

accept every volt

1

(c) as one increases so does the other

or

directly proportional

or

positive correlation

accept a numerical description, eg when one doubles the other also doubles

1

[7]**25**

(a) (i) circuit not complete

*accept circuit is broken**accept switch / s are open / off*

1

(ii) 9

allow 1 mark for correct substitution, ie 0.5×18 provided no subsequent step shown

2

(iii) 36

1

(b) can be switched on / off from top or bottom of stairs

1

(c) (i) (electric) shock

*accept fitting becomes live**accept answers giving a possible consequence of electric shock, eg death*

1

(ii) connect the earth wire

1

[7]**26**

(a) (i) also double

increases is insufficient

1

(ii) variable resistor*accept rheostat / potentiometer*

1

- (b) (i) the data / results / variables are continuous
accept data / results / variables are not categoric / discrete 1
- (ii) misreading the ammeter
do not accept misreading the meter / results
do not accept misreading the ammeter and / or voltmeter
reading / human error is insufficient 1
- (iii) straight line from the origin drawn passing close / through
points at 1 V, 5 V, 6 V and ignoring anomalous point
do not accept line drawn 'dot-to-dot' 1
- (iv) yes
mark is for the reason
- supports prediction
or
(straight) line passes through the origin
accept a mathematical argument, eg when p.d. went from 2 to 4 the
current went from 0.3 to 0.6
it's directly proportional is insufficient 1

[6]

27

- (a) (i) (connect) 30 (cells) 1
- in series 1
- (ii) current always flows in the same direction
or
current only flows one way 1
- (iii) 36 000
allow 1 mark for correctly converting 2 hours to 7200 seconds
answers 10 or 600 score 1 mark 2
- coulombs / C
do not accept c 1

(b) (i) 2160

*allow 1 mark for correct substitution, ie $\frac{1}{2} \times 120 \times 6^2$
answers of 1620 or 540 score 1 mark*

2

(ii) reduce it

1

any **one** from:

- draws a larger current (from battery)
- motor draws greater power (from battery)
*accept energy per second for power
accept more energy needed to move the bicycle*
- greater resistance force (to motion) / air resistance / drag / friction
*accept less streamlined
more mass to carry is insufficient*

1

[10]**28**

(a) (i) 4.5

1

(ii) 2.25 or their (a)(i) $\div 2$ correctly calculated

1

(iii) V_2

1

(b) (i) 30

1

(ii) 8

*allow 1 mark for correct substitution
ie 0.4×20
allow 1 mark for answers of 4 or 12*

2

(iii) **Y**

1

[7]**29**

(a) diode

accept LED

1

- (b) all symbols correct
must include at least voltmeter and diode

1



allow ecf from part (a) if the component is not identified as a diode
allow symbol without the line through triangle
ignore polarity of diode

voltmeter in parallel with component added in series

any additional components must not affect the ability to measure V
and I for the diode / their (a)

1

- (c) (i) 0.05

accept 50 mA

accept between 0.048 and 0.050 inclusive

1

- (ii) 16

$$\frac{0.8}{0.05}$$

their (c)(i) correctly calculated gains both marks

allow 1 mark for correct transformation and substitution

$$\frac{0.8}{0.05} \text{ or } \frac{0.8}{\text{their (c)(i)}}$$

allow 17 if using 0.048

2

[6]

30

- (a) (i) 0.25 (A)

1

- (ii) 75

allow 1 mark for converting 5 minutes to 300 seconds

or allow 1 mark for correct substitution

$$\text{ie } 0.25 \times 300$$

allow 1 mark for an answer 1.25

allow 1 mark only for their (a)(i) $\times 300$ correctly calculated

2

coulombs or C

do **not** accept c

1

(b) any **two** from:

- fault not repaired
accept if a fault was to occur
- larger current will (still) flow
- aluminium foil will not melt (if a fault)
accept aluminium foil needs a higher current / charge to melt
- wiring will overheat / (may) cause a fire
accept idea of fire hazard
*do **not** accept explode etc*

2

[6]**31**

(a) fleece rubs against shirt

it refers to the fleece

1

or

friction (between fleece and shirt)

(causing) electrons to transfer from one to the other

accept a specific direction of transfer

*do **not** accept charge for electrons*

positive electrons negates this mark

movement of protons negates this mark

1

(b) Electrical charges move easily through metals.

1

An electric current is a flow of electrical charge.

1

(c) (i) copper

reason only scores if copper chosen

1

(good electrical) conductor

accept it is a metal

any mention of heat conduction negates this mark

1

(ii) lower than

1

(iii) accept any sensible suggestion, eg:

- too many variables (to control)
 - lightning strikes / storms are random / unpredictable
 - do not know which building will be struck
 - do not know when a building will be struck
 - do not know when lightning will happen
 - (very) difficult to create same conditions in a laboratory
 - lightning storms are not the same
- it is not safe is insufficient*
*do **not** accept lightning does not strike the same place twice*

1

[8]**32**

(a) brown

1

(b) outside / case is plastic / an insulator

- accept is double insulated*
accept non-conductor for plastic
*do **not** accept it / hairdryer is plastic*

1

(c) (i) (1) S_1

and no other

1

(2) S_1 and S_3

both required, either order

1

(ii) S_1 must be ON (for either heater to work)

*do **not** accept reference to 'fan' switch*

1

S_1 switches the fan on

1

(d) 1495

*allow **1** mark for correct substitution*
ie, 6.5×230

2






watt(s) or W

*an answer of 1.495 kW gains 3 marks**although the unit is an independent mark for full credit**the unit and numerical value must be consistent**accept joules per second or J/s*

1

[9]

33

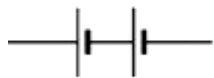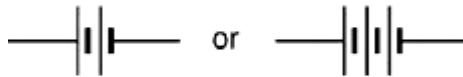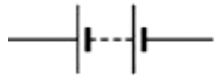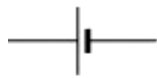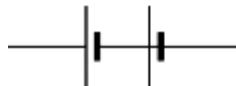(a) (i) ammeter and battery **in series** with the **gauge***symbols must be correct**ignore a voltmeter drawn in series***accept****not***or cells reversed to cancel out*

1

voltmeter in parallel with the gauge

*symbol must be correct**accept a freestanding circuit**diagram provided strain gauge is labelled or a resistor symbol used for the strain gauge*

1

(ii) d.c. flows only in one direction

a.c. changes direction is insufficient

1

(b) (i) 75

*this answer only**allow 1 mark for correct substitution **and** transformation,*

$$\text{ie resistance} = \frac{3.0}{0.040}$$

2

(ii) increases

1

(iii) elastic / strain potential*do **not** accept potential*

1

[7]**34**

(a) switch

allow answer circled in box

1

(b) 24

1

(c) equal to 0.25 A

1

(d) 4

1

[4]**35**

(a) a light-dependent resistor

1

(b) any **three** from:

- resistance starts at 500 (kilohms)
- (resistance) falls rapidly as intensity increases from 0
accept resistance falls
accept brightness for intensity
- (resistance) halves between 10 and 20 lux
- (resistance) falls slightly between 20 and 50 lux
or
- (resistance) almost constant / levels out between 20 and 50 lux
- at 50 lux, resistance = 10 (kilohms)
for full credit the word resistance must be used correctly at least once
an answer resistance falls as intensity increases gains 2 marks - this may be combined with one of the bullet point marks for full credit

3

(c) (i) decrease

1

- (ii) resistance increases
this can score without (c)(i)

1

(d) A circuit to switch on security lighting when it gets dark.

1

[7]**36**

(a) (i) light dependent resistor / LDR
accept ldr

1

- (ii) 25 (kilohms)
accept 24 - 26 inclusive
accept 25 000 Ω

1

- (iii) 5 (V) or their (a)(ii) correctly converted to ohms $\times 0.0002$ correctly calculated

allow 1 mark for converting 25 k Ω /

their (a)(ii) to ohms

or

allow 1 mark for correct substitution

ie $0.0002 \times 25(000)$

or $0.0002 \times$ their (a)(ii)

allow an incorrect conversion from kilohms providing this is clearly shown

2

- (b) (i) linear scale

using all of the available axis

must cover the range 4 - 6 v

or their (a)(iii) - 6 v and lie within the range 0 - 15 inc.

1

- (ii) negative gradient line

*do **not** allow lines with both positive and negative gradients*

1

passing through 20 lux and their (a)(iii)

only scores if the first mark is awarded

only scores if line does not go above 6 volts

1

- (c) (i) 37.5 (k Ω) or their (a)(ii) + 50 % (a)(ii) correctly calculated

1

- (ii) light intensity value would be unreliable / not accurate

1

due to variation in resistance value

accept because resistance varies by ± 50 %

accept tolerance of resistor is too great


*do **not** accept results are not accurate*

1

[10]

37

(a)

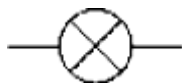

accept 'the humpback bridge' symbol

accept circle with cross but no lines

if more than one symbol drawn, no mark unless lamp is labelled

1

(b) (i) 24

allow 1 mark for correct substitution ie $\frac{2800}{120}$

allow 1 mark for an answer 1440

ignore any unit

2

(ii) watt

1

(c) larger than

accept correct indication inside the box

accept an answer meaning larger than ie greater than

1

[5]