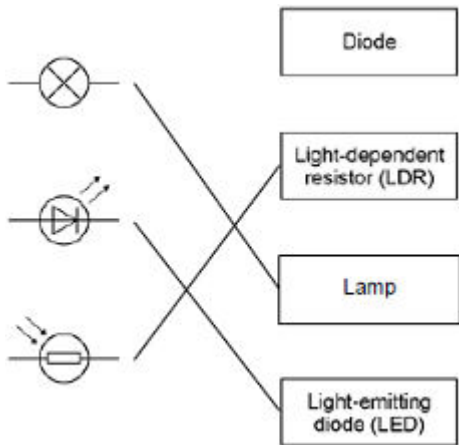


Mark schemes

1	(a) $V = 0.10 \times 45$	1
	4.5 (V)	1
	(b) $R = 12 / 0.10$	1
	total resistance = 120 (Ω)	1
	$R = 120 - 105 = 15$ (Ω)	1
	(c) (total) resistance decreases	1
	(so) current increases	1
		[7]

2

(a)



allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii) V_1

1

(c) (i) potential difference / voltage of the power supply

accept the power supply

accept the voltage / volts

accept number of cells / batteries

accept (same) cells / batteries

do not accept same ammeter / switch / wires

1

(ii) bar drawn – height 1.(00)A

ignore width of bar

allow 1 mark for bar shorter than 3rd bar

2

(iii) as the number of resistors increases the current decreases

1

[10]

3

(a) 35

an answer with more than 2 sig figs that rounds to 35 gains 2 marks

allow 2 marks for correct method, ie $\frac{230}{6.5}$

allow 1 mark for $I = 6.5$ (A) or $R = \frac{230}{26}$

an answer 8.8 gains 2 marks

an answer with more than 2 sig figs that rounds to 8.8 gains 1 mark

3

- (b) (maximum) current exceeds maximum safe current for a 2.5 mm² wire
accept power exceeds maximum safe power for a 2.5 mm² wire

or

- (maximum) current exceeds 20 (A)
(maximum) current = 26 (A) is insufficient

1

- a 2.5 mm² wire would overheat / melt
accept socket for wire
*do **not** accept plug for wire*

1

- (c) a.c. is constantly changing direction
accept a.c. flows in two directions
accept a.c. changes direction
a.c. travels in different directions is insufficient

1

- d.c. flows in one direction only

1

[7]

4

- (a) (i) 6

1

- (ii) variable resistor

1

- (iii) voltmeter

1

- (b) (i) point at 3 V ringed

1

- (ii) The student misread the ammeter.

1

- (iii) 1 (volt)

accept every volt

1

- (c) as one increases so does the other

or

directly proportional

or

positive correlation

accept a numerical description, eg when one doubles the other also doubles

1

[7]