

Question 7		
(a) (i)	work (done)/energy (supplied) per unit charge (by battery) ✓ (or pd across terminals when no current passing through cell or open circuit)	1
(a) (ii)	when switch is closed a current flows (through the battery) ✓ hence a pd/lost volts develops across the internal resistance ✓	2
(b)	(use of $\epsilon = V + Ir$) $I = 5.8/10 = 0.58 \text{ (A)}$ ✓ $6.0 = 5.8 + 0.58r$ ✓ $r = 0.2/0.58 = 0.34 \text{ (}\Omega\text{)}$ ✓	3
(c)	need large current/power to start the car ✓ (or current too low) internal resistance limits the current/wastes power(or energy)/reduces terminal pd/increases lost volts ✓	2
Total		8

Question 7		
a	i	(use of $V = IR$) $R_{\text{total}} = 1 \text{ (ohm)} \checkmark$ $V = 1 \times 1 = 1.0 \text{ V} \checkmark$ 2
a	ii	(use of $V = IR$) $R = 9.0/1.0 = 9.0 \Omega \checkmark$ $r = 9.0 - 1.0 - 6.0 = 2.0 \Omega \checkmark$ or use of $(E = I(R + r))$ $9.0 = 1(7 + r) \checkmark$ $r = 9.0 - 7.0 = 2.0 \Omega \checkmark$ 2
a	iii	(use of $W = VIt$) $W = 9.0 \times 1.0 \times 5 \times 60 \checkmark$ $W = 2700 \text{ J} \checkmark$ 2
a	iv	energy dissipated in internal resistance = $1^2 \times 2.0 \times 5 \times 60 = 600 \text{ (J)} \checkmark$ percentage = $100 \times 600/2700 = 22\% \checkmark$ CE from part aii 2
b		internal resistance limits current \checkmark hence can provide higher current \checkmark or energy wasted in internal resistance/battery \checkmark less energy wasted (with lower internal resistance) \checkmark or charges quicker \checkmark as current higher or less energy wasted \checkmark or (lower internal resistance) means higher terminal pd/voltage \checkmark as less pd across internal resistance or mention of lost volts \checkmark max 2
		Total 10
		UMS conversion calculator www.aqa.org.uk/umsconversion

6	a	i	(use of $P=VI$) $I = 36/12 + 6/12 \checkmark = 3.5 \text{ (A)} \checkmark$	2
6	a	ii	(use of $V=IR$) $R = 12/3 = 4 \text{ (}\Omega\text{)} \checkmark$	1
6	a	iii	$R = 12/0.50 = 24 \checkmark \text{ (}\Omega\text{)}$	1
6	b		terminal pd/voltage across lamp is now less OR current is less \checkmark due to lost volts across internal resistance OR due to higher resistance \checkmark lamps less bright \checkmark	3
6	c	i	current through lamps is reduced as resistance is increased or pd across lamps is reduced as voltage is shared \checkmark hence power is less OR lamps dimmer \checkmark	2
6	c	ii	lamp Q is brighter \checkmark lamp Q has the <u>higher resistance</u> hence <u>pd/voltage</u> across is greater \checkmark current is the same for both \checkmark hence power of Q greater \checkmark	max 3

Mark schemes

1

- (a) power increases to a maximum / (up) to 3.0 (2.8 -3.4) Ω / / (up)to 3.0 W ✓
then decreases ✓

2

- (b) (i) (use of $P = I^2 R$)
when $R = 0.8 \Omega$ power = 1.95 W ✓
 $1.9 = I^2 \times 0.8$ ✓
 $I = \sqrt{2.375} = 1.5(4)$ (A) ✓
Range
1.9 - 2.0 W for power (first mark)
Current 1.5 – 1.6 A

3

- (ii) (use of $V = IR$)
 $V = 1.54 \times 0.8$ ✓
 $V = 1.2$ V ✓
CE from part (i)

2

- (iii) (use of $\varepsilon = V + Ir$)
 $6.0 = 1.2 + 1.54 \times r$ ✓
 $r = (6.0 - 1.2) / 1.54 = 3.1$ (2.9 – 3.2) (Ω) ✓
use of maximum power theorem (quoted) as alternative method can get both marks i.e. read peak maximum from graph
CE from part (ii)

2

- (c) power would decrease (as R increased) ✓
pd / voltage across R is now constant / equal to emf ✓
and so power proportional to $1 / R$ / inversely proportional to R OR
can quote $P = V^2 / R$ but only if scored second mark ✓

3

[12]

Mark schemes

1

- (a) emf is the work done / energy transferred by a voltage source / battery / cell ✓per unit charge✓

OR

electrical energy transferred / converted / delivered / produced✓

per unit charge✓

OR

pd across terminals when no current flowing / open circuit✓✓

not in battery

accept word equation OR symbol equation with symbols defined if done then must explain energy / work in equation for first mark

2

- (b) (i) by altering the (variable) resistor✓

1

- (ii) reference to correct internal resistance✓

e.g. resistance of potato (cell)

terminal pd = emf – pd across internal resistance / lost volts✓

pd / lost volts increases as current increases OR as (variable)

resistance decreases greater proportion / share of emf across internal resistance✓

accept voltage for pd

3

- (iii) draws best fit straight line and attempts to use gradient✓

uses triangle with base at least 6 cm✓

value in range 2600 – 2800 (Ω)✓

3

stand-alone last mark

- (c) total emf is above 1.6 V✓

but will not work as current not high enough / less than 20 mA✓

2

[11]

Question	Answer	Marks	Guidance
3 (a) (i)	energy transferred from source/changed from some form to electrical energy; per unit charge (to drive charge round a complete circuit)	M1 A1	allow energy <u>divided by</u> charge
(ii)	any source has an <u>internal resistance</u> where energy is transferred into thermal energy /lost as heat	B1 B1	there will be 'lost' volts (across the cell when a current is drawn) or $V = E - Ir$ explained
(b) (i)	$V = IR$ $1.2 = 0.2 R$ $R = 6.0 \Omega$	C1 A1	substitution needed to score mark allow 6Ω
(ii)	$1.6 - 1.2 = 0.4 = 0.2 r$ $r = 2.0 \Omega$	C1 A1	allow 2Ω
(c) (i)1	$Q = It = 0.20 \times 3600 \times 1.5$ $= 1100$ correct unit,	C1 A1 B1	substitution needed to score mark 1080 allow 1 mark max for 0.3 or 18 allow C, kC, A s exception 0.3 A h or 18 A min scores 3 marks
(i)2	energy = $QV = 1100 \times 1.2$ or $I^2Rt = 0.2^2 \times 6 \times 5400$ $= 1320$ (J)	C1 A1	ecf (c)(i)1 substitution needed to score mark 1296(1080) allow 1 mark for 1728 (using 1.6)
(ii)	I is constant for about 9 to 10 hours because <u>internal</u> resistance remains constant/cell operates at constant <u>emf</u> I falls <u>rapidly/towards zero</u> over last hour or so because <u>cell's/chemical energy</u> is used up (so E falls)	B1 B1 B1 B1	QWC must have link between observation and reason to score full marks accept r of cell increases causing fall in V or I
Total		17	

Question	Answer	Marks	Guidance
4 (a)	R's in parallel have same V/AW so $4.0 \times 0.30 = 6.0 \times 0.20$	M1 A1	allow I splits in inverse ratio to R or AW; hence I in 6 ohm = $4 / 6 \times 0.3 = 0.2$ A
(b) (i)	sum of/total current into a junction equals the sum of/total current out or total algebraic sum of currents is zero	B1	allow Kirchhoff's first law
(ii)	0.50 (A)	A1	accept 0.5 (A) (no SF error)
(c)	correct formula for R_p and substitution $R_p = 2.4 \Omega$ $R_s = 8.0 (\Omega)$	C1 C1 A1	apply ecf to R_p for second mark accept 8 (Ω) (no SF error)
(d) (i)	energy transferred from source/changed from some form to electrical energy; <u>per</u> unit charge (to drive charge round a complete circuit)	M1 A1	allow form as e.g. light/chemical/heat allow energy <u>divided by</u> charge
(ii)	$V = IR = 0.50 \times 8.0 = 4.0$ (V)	A1	ecf b(ii),c i.e. answer = b(ii) x c accept 4 (V) (no SF error)
(iii)	$E - V = Ir$ giving $5.0 - 4.0 = 0.50 r$ $r = 2.0 (\Omega)$	C1 A1	ecf b(ii) accept 2 (Ω) (no SF error); give max of 1 mark for $r = 3.3 \Omega$, i.e. using $I = 0.3$ A
Total		12	

